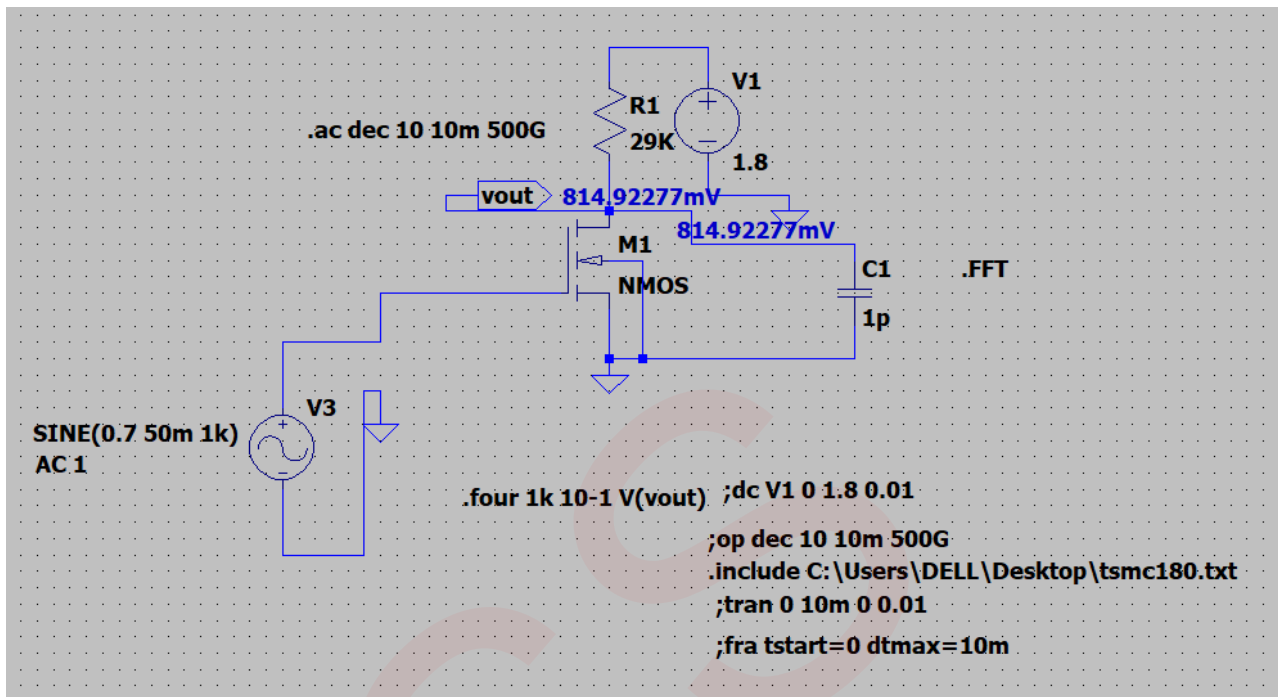


- Design an NMOS input resistive loaded CS amplifier such that the small signal DC gain is anywhere between 5 to 15 (Excluding 5 and 15). The input DC bias voltage is 0.7 V. The output DC voltage can be anywhere between 0.7 V and 1.2 V. Perform the following experiments on the designed amplifier.

For gain to become 5.4 and output voltage to become 0.814 volt. The size of a mos device is taken as $W=0.55\mu$ and $L=0.18\mu$



```

UNKNOWN CONTROL CARD
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM3 MOSFETS ---

Name:      m1
Model:     nmos
Id:        3.40e-05
Vgs:       7.00e-01
Vds:       8.15e-01
Vbs:       0.00e+00
Vth:       4.67e-01
Vdsat:     1.44e-01
Gm:        2.35e-04
Gds:       8.49e-06
  
```

Drain current comes out to be = $34\mu\text{A}$

Small signal AC analysis(.AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic: ☒

DC offset[V]:

Amplitude[V]:

Freq[Hz]:


Tdelay[s]:

Theta[1/s]:

Phi[deg]:

Ncycles:

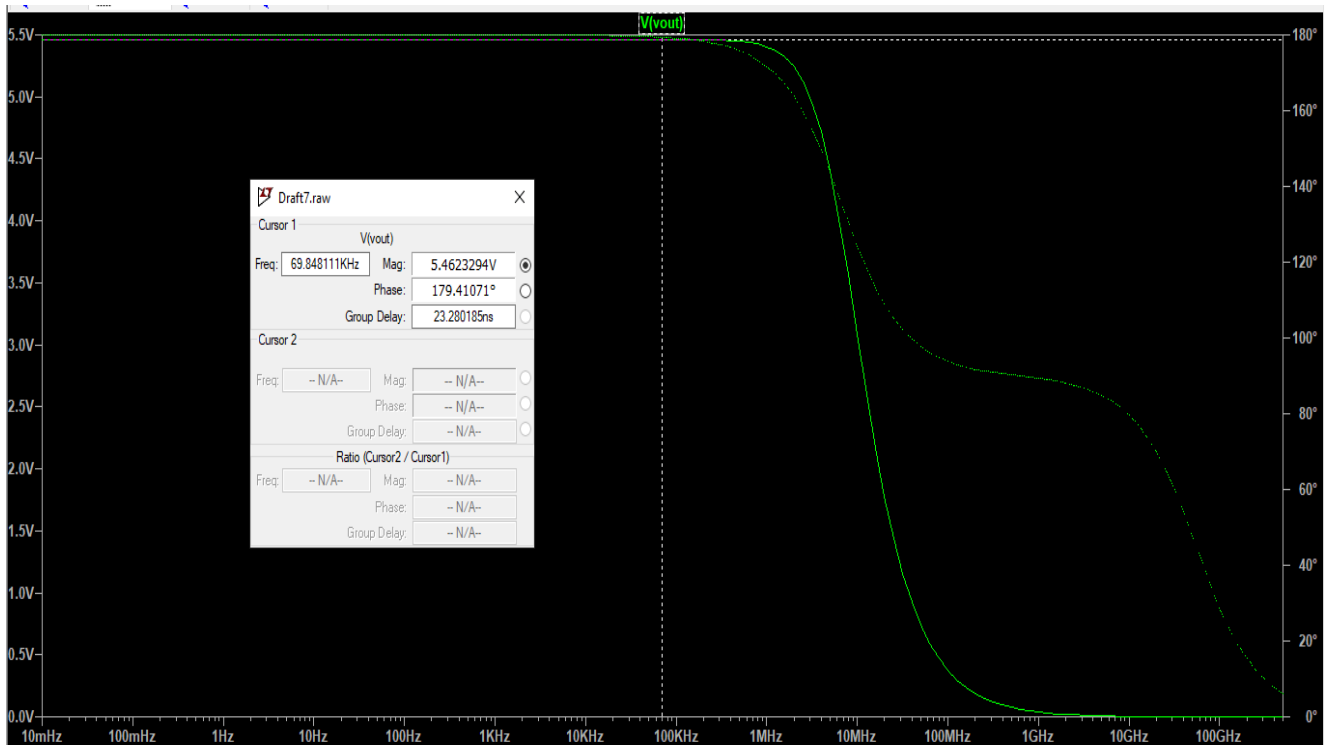- Frequency response of the amplifier. Find the small signal DC gain and bandwidth of the amplifier. Compare it with calculated value using the small signal parameters obtained from the DC operating point simulation. Also find the bandwidth of the amplifier.



Calculated gain-

$$R_D = 29K$$

$$r_0 = \frac{1}{G_{ds}}$$

$$r_0 = \frac{1}{8.49e-06} = 117.785k$$

$$R_D || r_0 = 23.27k$$

$$A_v = g_m (R_D || r_0)$$

$$A_v = 2.35 \times 10^{-4} \times 23.27 k = 5.4$$

Fig 1 – Gain in simulation

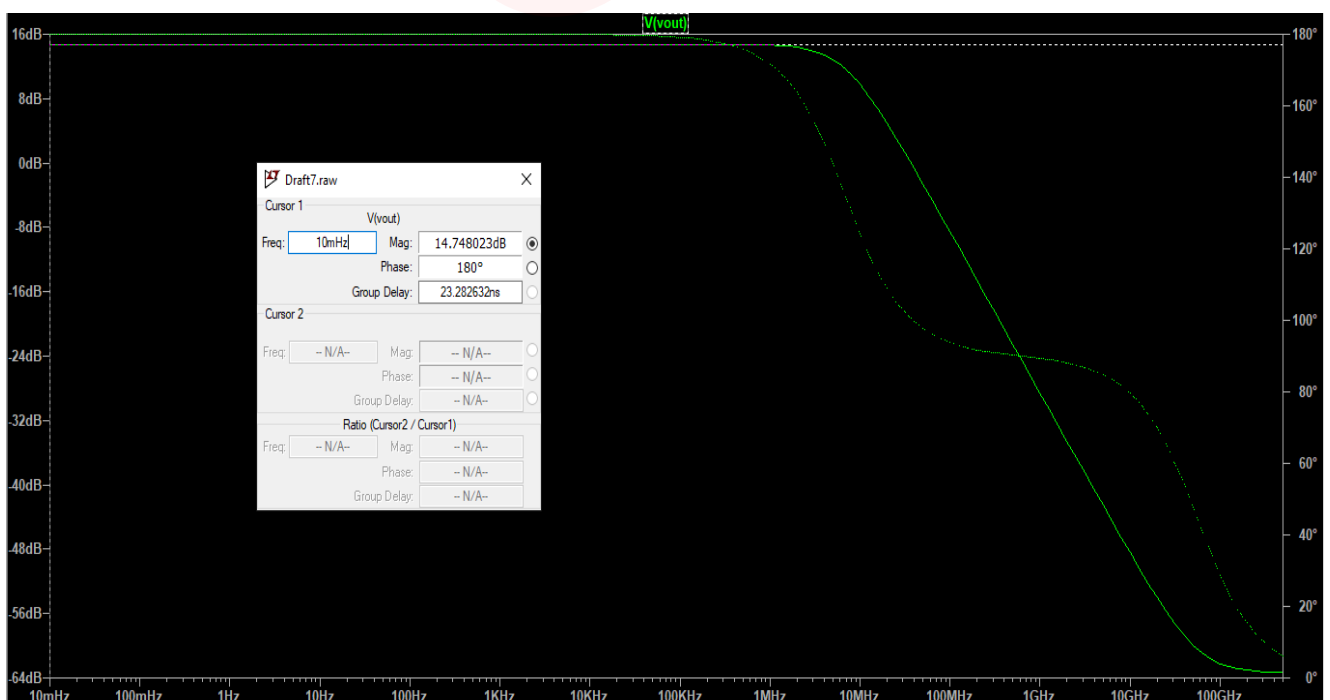
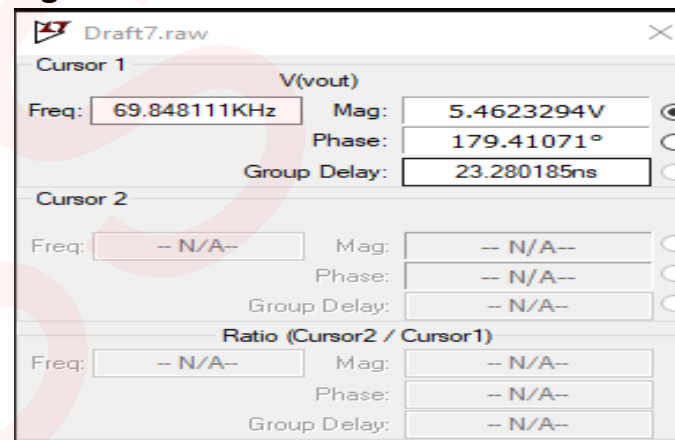


Fig -2 (Gain in decibel)


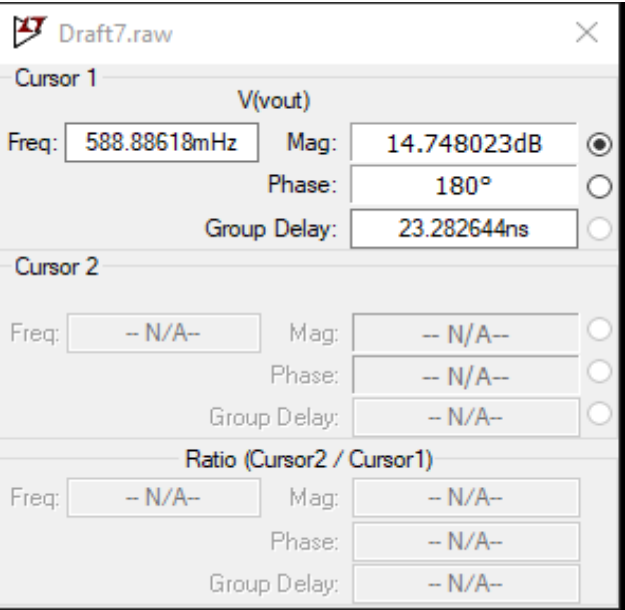


Fig -3 (Corresponding frequency)

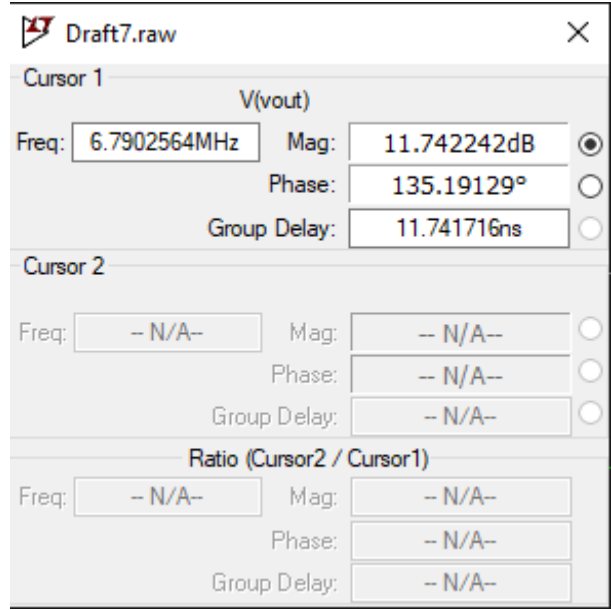

For bandwidth:

$A_v = 20 \log(\text{gain})$

$= 20 \log(5.4) = 14.64 \text{ Decibel}$

For Bandwidth: (Simulation)

$\text{Gain in Db} - 3\text{dB} = 14.74 - 3 = 11.74 \text{ dB}$


For 11.74 decibel the frequency is 6.79 MHz

$\text{Bandwidth} = f_1 - f_2 = 6.79 - 0 = 6.79 \text{ MHz}$


Parameter	Calculated	Simulation
Gain	5.4	5.46 (Fig 1)
Gain in dB	14.64dB	14.74 dB (Fig 2)
Bandwidth	6.94 MHz	6.79 MHz (Fig 3)

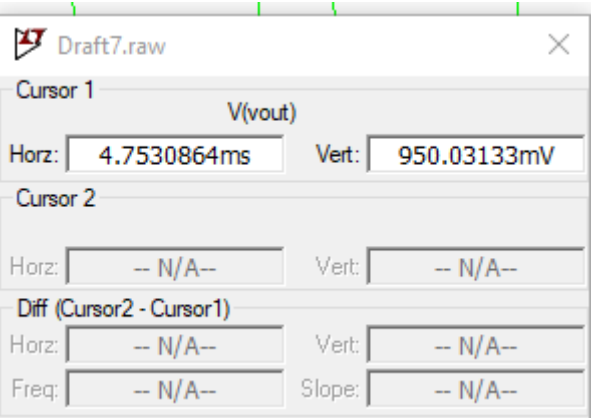b) Excite the amplifier with a 50 mV peak-to-peak sine wave of frequency 1 kHz riding on the input DC bias voltage and obtain the output. What is the peak-to-peak voltage of the output?

- Here frequency is given as 1 KHz , DC offset is 0.7 V , Amplitude = 25 millivolt



Maximum value of output voltage

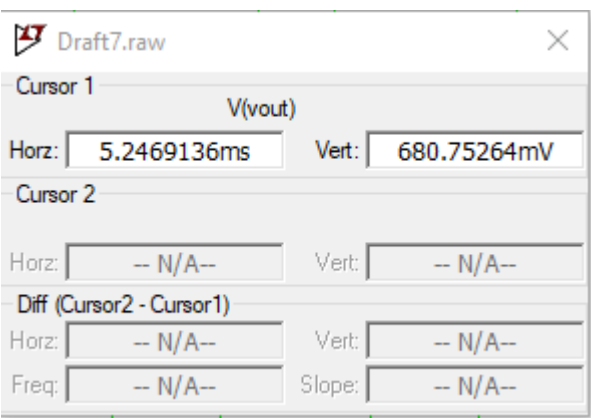

Minimum value of Output voltage

For output-

$$V_{(\max)} = V(\text{dc}) + V_m \quad V_{(\min)} = V(\text{dc}) - V_m \quad \text{Adding this two-}$$

$$V_m(\text{out}) = [V_{(\max)} - V_{(\min)}] / 2$$

$$V_m(\text{out}) = [950 \text{ mV} - 680.7 \text{ mV}] / 2 = 134.65 \text{ mV}$$

Peak to peak voltage of output = 269.3 mV


For input-

$$V_{(\max)} = V(\text{dc}) + V_m \quad V_{(\min)} = V(\text{dc}) - V_m \quad \text{Adding this two-}$$


$$V_m(\text{in}) = [V_{(\max)} - V_{(\min)}] / 2$$

$$V_m(\text{in}) = [724.816 \text{ mV} - 675.09 \text{ mV}] / 2 = 24.86 \text{ mV}$$

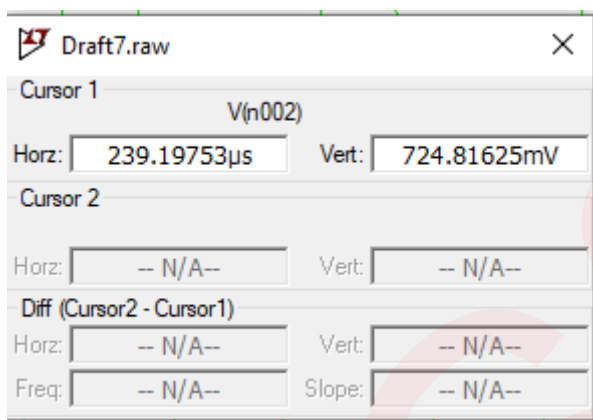
$$\text{Gain} = \frac{\text{output voltage}}{\text{input voltage}} = \frac{134.65 \text{ mV}}{24.86 \text{ mV}} = 5.4 \text{ which is exactly same as calculated earlier}$$



Maximum Value of input voltage

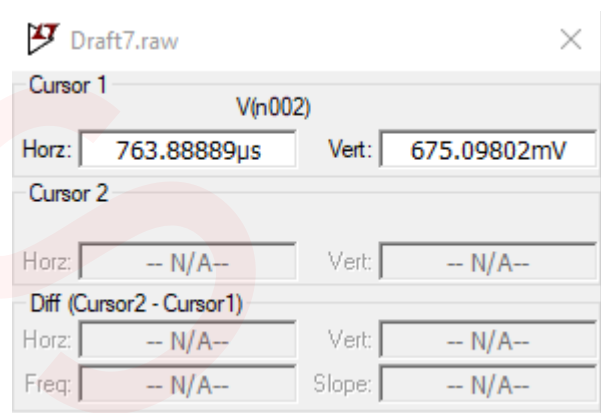


Minimum value of input voltage

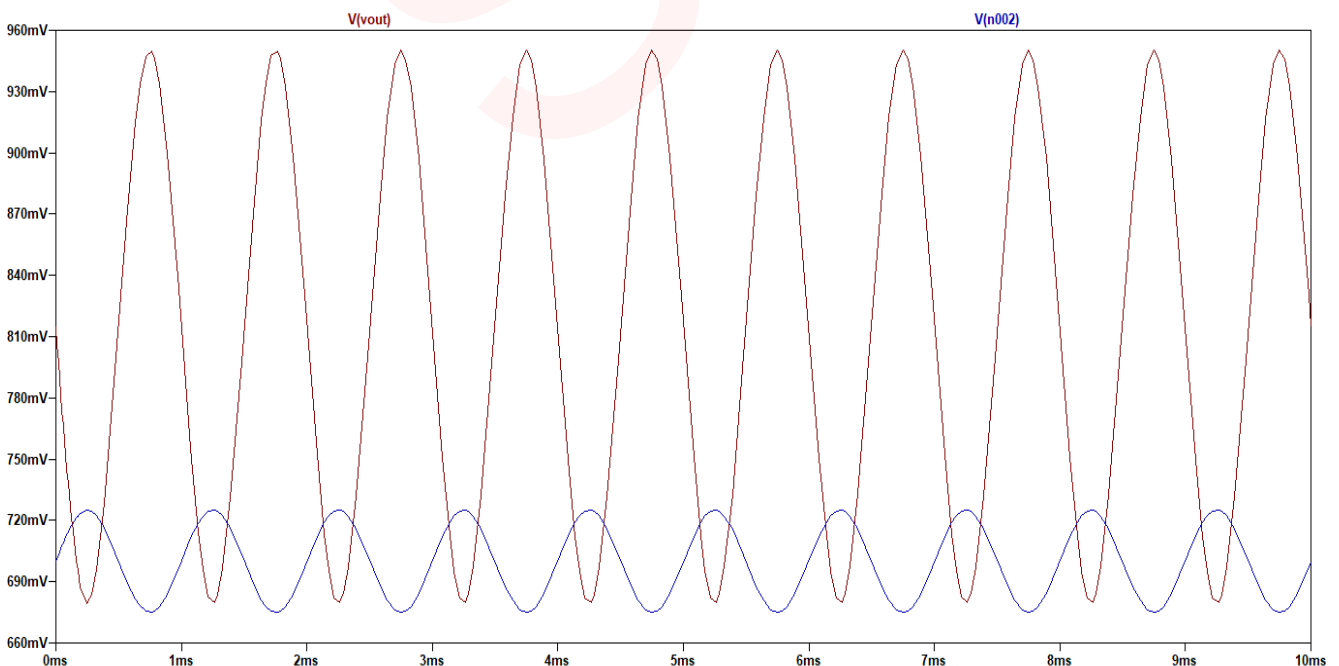

Peak to peak voltage of output = 269.3 mV


c) Repeat the transient analysis by increasing the input to 100 mVpp, 200 mVpp and 500 mVpp. Obtain the output and note down the peak-to-peak voltage. What do you observe and why?

For 100 mv peak to peak input:

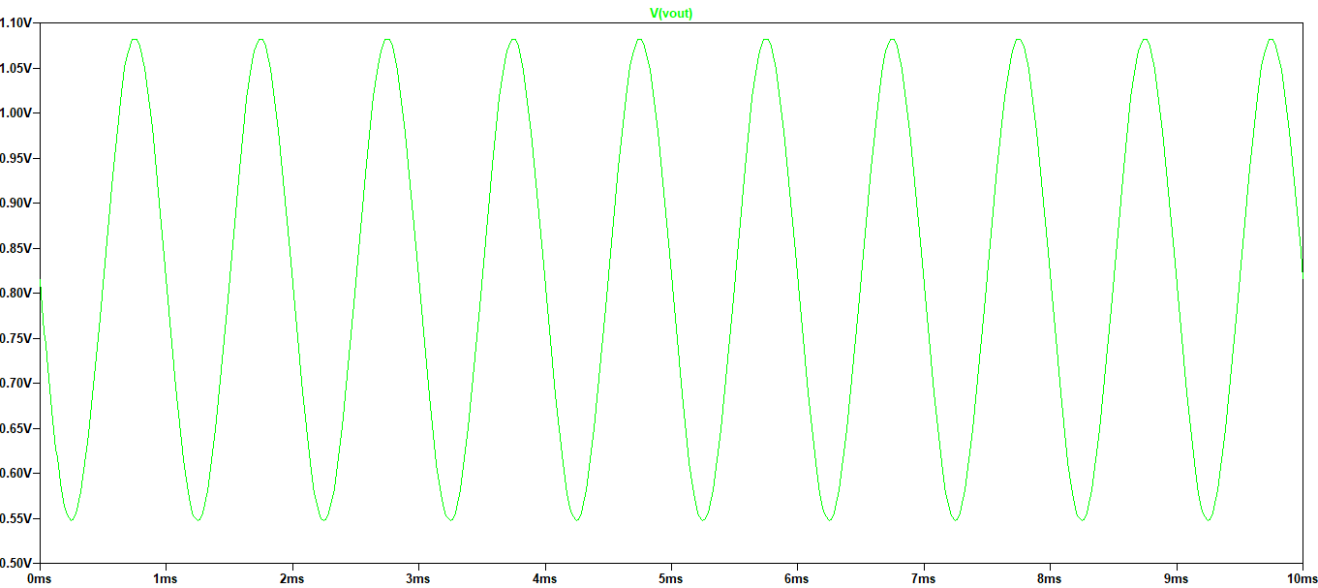


Output voltage peak to peak- $1.08 - 0.548 = 0.532$ volt, $V_m = 266$ mV

For 200 mv peak to peak input:

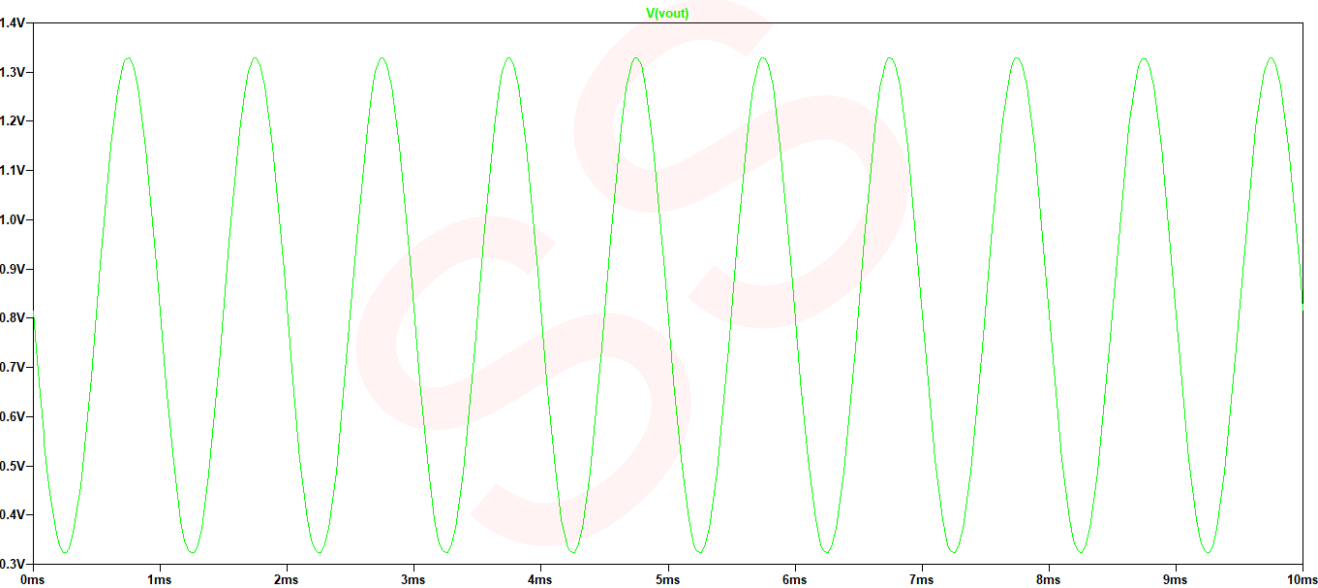

Output voltage peak to peak- $1.32 - 0.323 = 0.997$ v , $V_m = 498.5$ mV

For 500 mv peak to peak input :

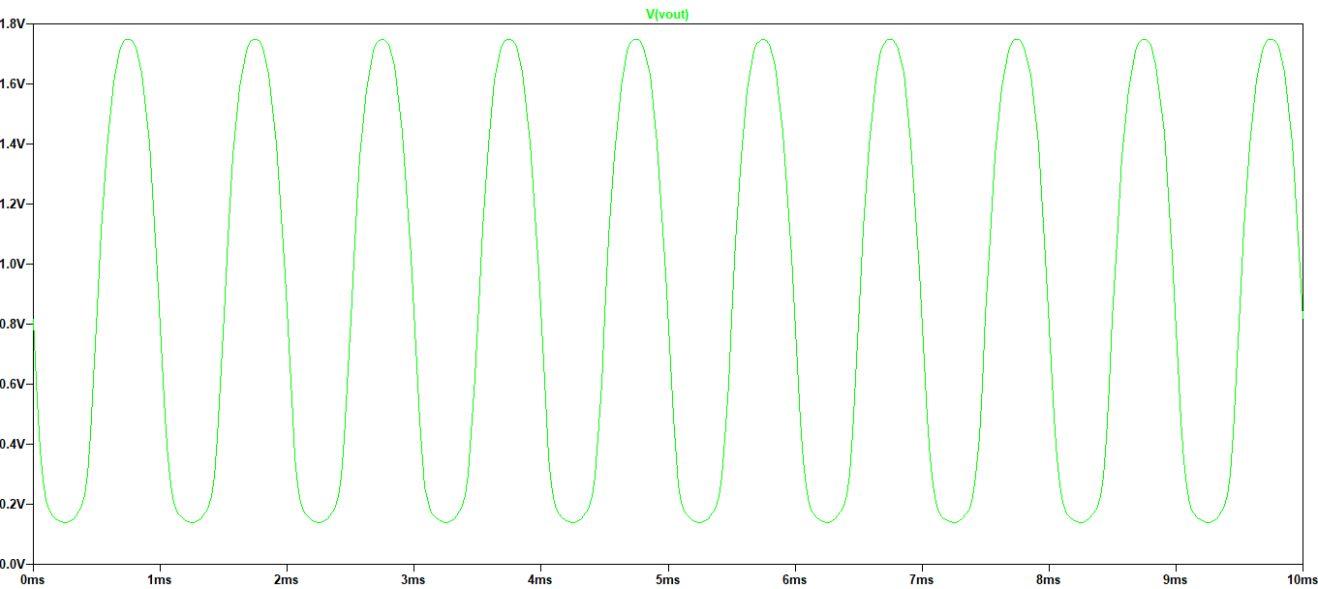

Output voltage peak to peak- $1.74 - 0.1398 = 1.6$ volt, $V_m = 800$ mv

Observation –

we increase the amplitude of sinusoidal signal

1)The peak to peak output increases.

2)Minimum value decreases


3)maximum value increases

The output begins to saturate at supply voltage because our output cannot go beyond supply voltage 1.8 volt.

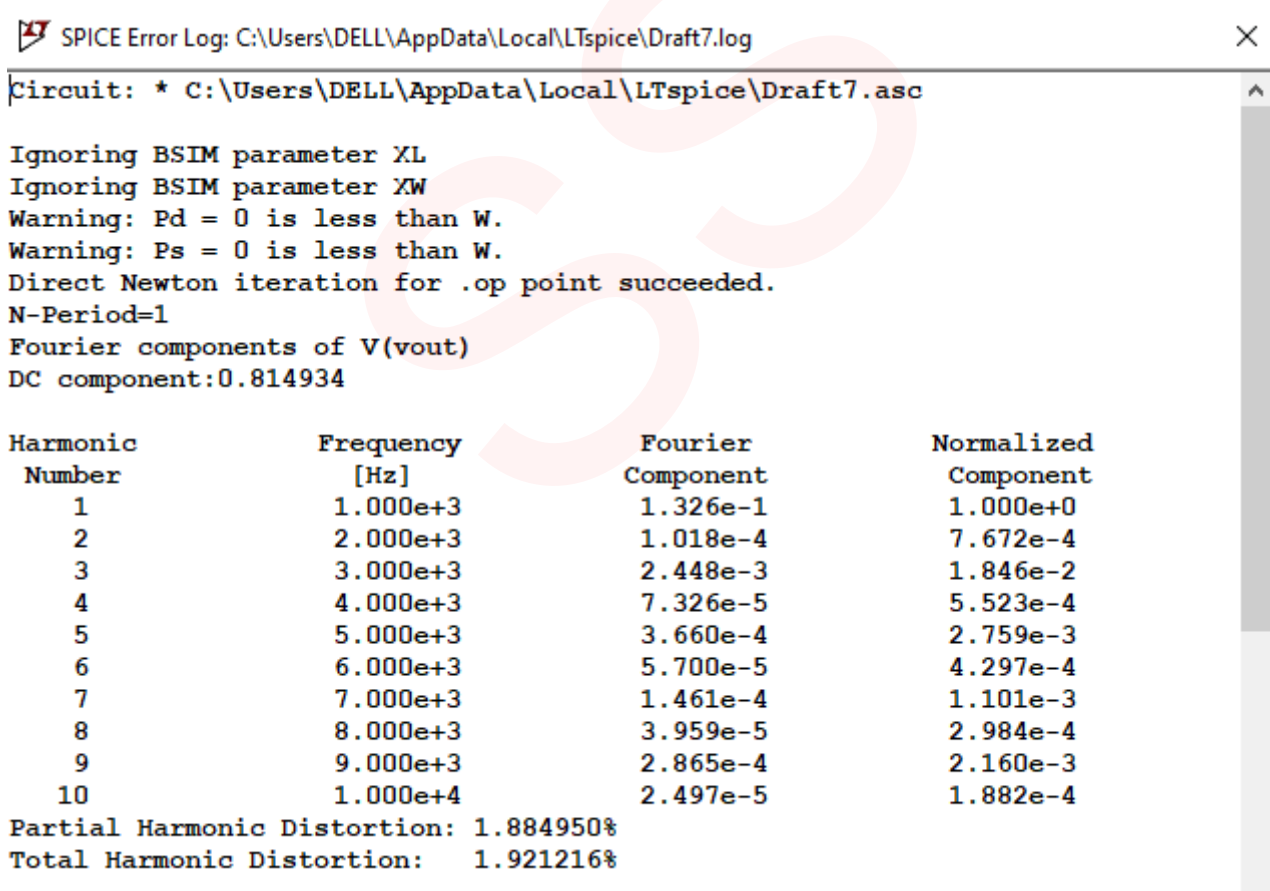(d) Find the 1-dB compression point of the designed amplifier by performing total harmonic distortion (THD) analysis.

$$\text{Fundamental component} = a_1 V_m + \frac{3}{4} a_3 V_m^3$$

$$\text{Third harmonic component} = \frac{1}{4} a_3 V_m^3$$



$$\text{Fundamental component} = a_1 V_m + \frac{3}{4} a_3 V_m^3 = 132.6 \text{ m A}$$

$$\text{Third harmonic component} = \frac{1}{4} a_3 V_m^3 = 2.448 \text{ mA}$$

1-dB compression point=

$$\sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

$$V_m = 25 \text{ mV}$$

By calculating I get - $a_3 = 626.68$, $a_1 = 5.01$

$$\text{1-dB compression point} = \sqrt{[0.145 * 5.01] / 626.68} = 0.034$$

2) Now the gain of the CS amplifier is required to be increased three folds without changing the main transistor and power supply. Retain the input and output DC voltages in the first CS amplifier. How will you modify the design? You are free to change the resistor, add any transistor and/or current source. Perform all the analysis mentioned in the first problem statement (above).

Gain obtained in first CS amplifier = 5.4
 Now three times = $5.4 \times 3 = 16.2$

$$\left(\frac{V_o}{V_{in}} \right) = A_v = g_m (R_D || r_o)$$

$$g_m (R_D || r_o) = 16.2$$

$$2.35 \times 10^{-4} \left(\frac{R_D \times 117.785 \text{ k}}{R_D + 117.785 \text{ k}} \right) = 16.2$$

$$\frac{R_D \times 117.785 \text{ k}}{R_D + 117.785 \text{ k}} = \frac{16.2}{2.35 \times 10^{-4}}$$

$$R_D + 117.785 \text{ k} = 1.7 R_D$$

$$0.7 R_D = 117.785 \text{ k} \Omega$$

$$R_D = 168.26 \text{ k} \Omega$$

Drain current in previous amplifier = $34 \mu\text{A}$, $V_{out} = 0.814 \text{ V}$

$$\therefore 34 \mu\text{A} = \frac{1.8 - 0.814}{168.26 \text{ k}} + I$$

$$34 \mu\text{A} = 5.85 \mu\text{A} + I$$

$$I = 28.15 \mu\text{A}$$


The drain current was $34 \mu\text{A}$ and voltage as 0.814 Volt .

We get new drain resistor as 168.26 Kohm for 3 times gain (5.4).


By above calculation based on 3 times gain as 16.2 we get addition current of $28.15 \mu\text{A}$

So we put current source as $28.15 \mu\text{A}$ parallel to drain resistor 168.26 K ohm

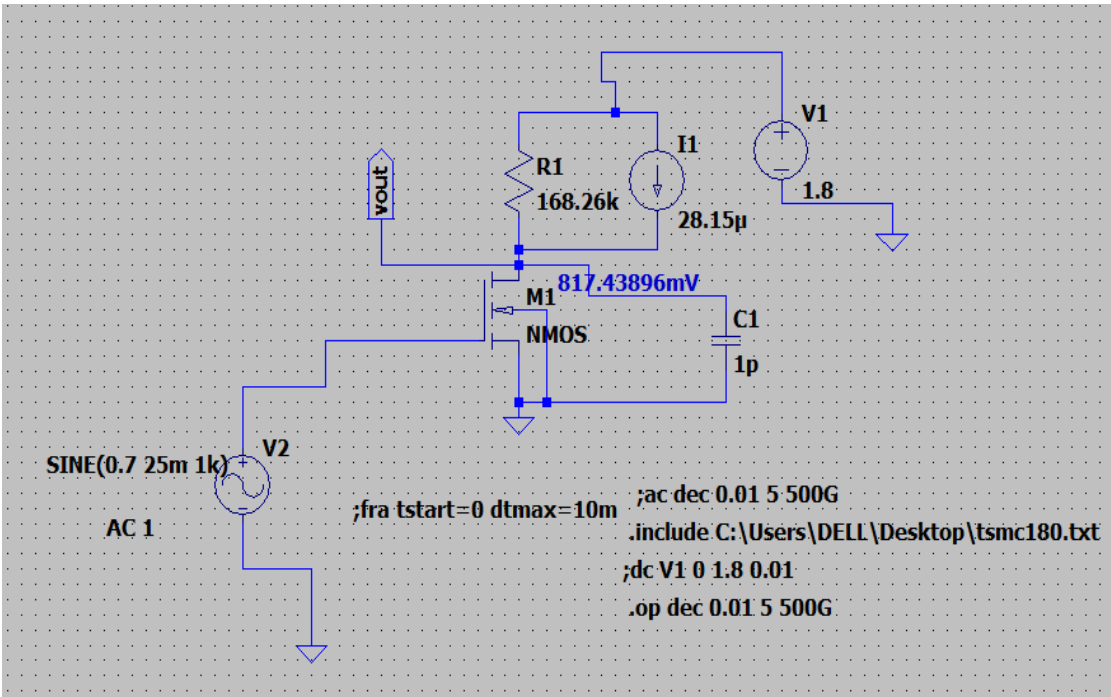The circuit with 28.15μA current source parallel to drain resistance is below.



a) Frequency response

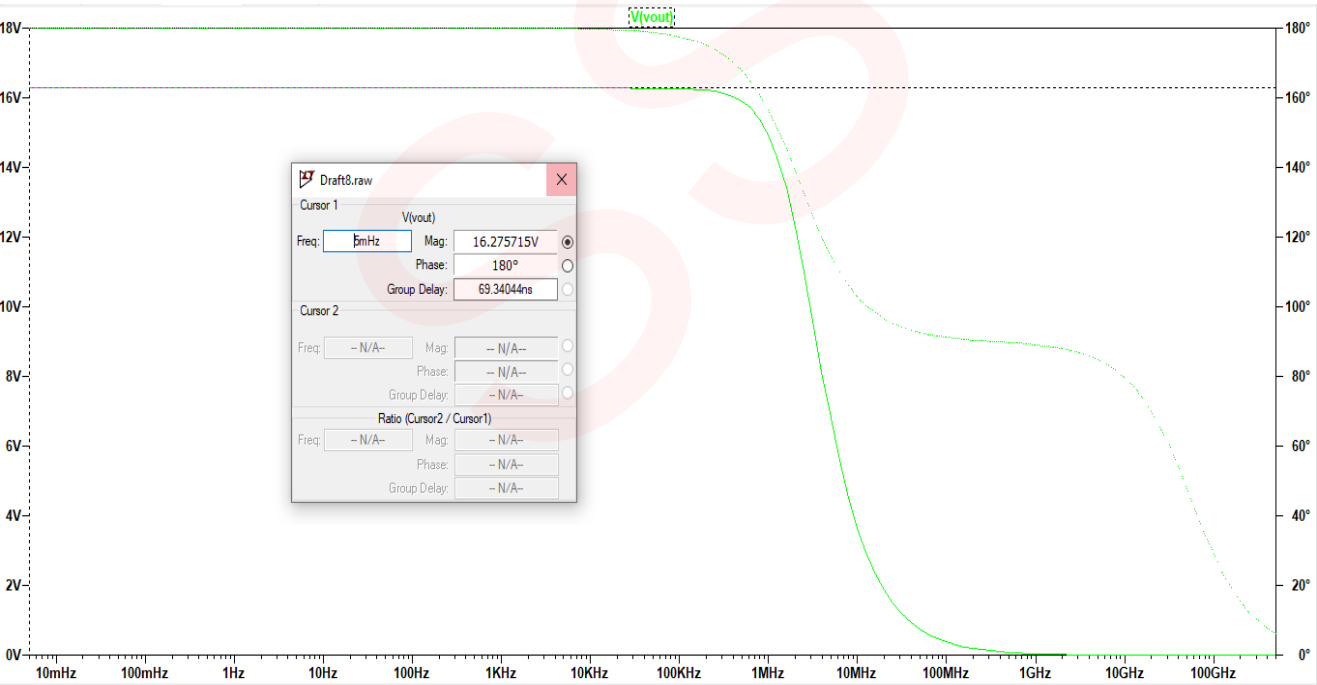

We can see in simulation also that our gain is 3 times that of previous gain which is 16.275


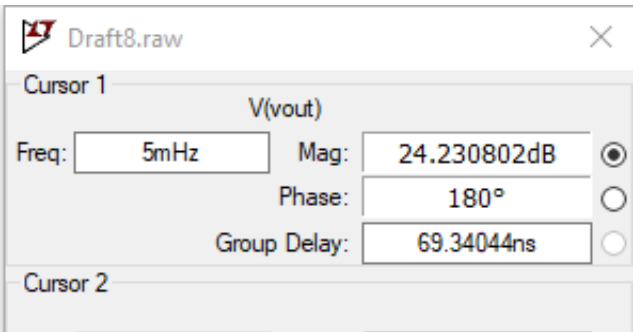



Fig 4

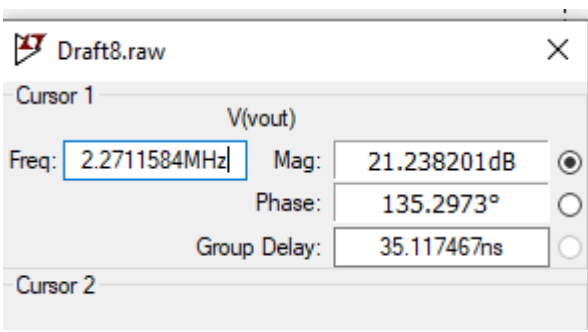

For bandwidth (Fig 5)

In db we get $20 \log 16.2 = 24.2\text{dB}$

In dB-

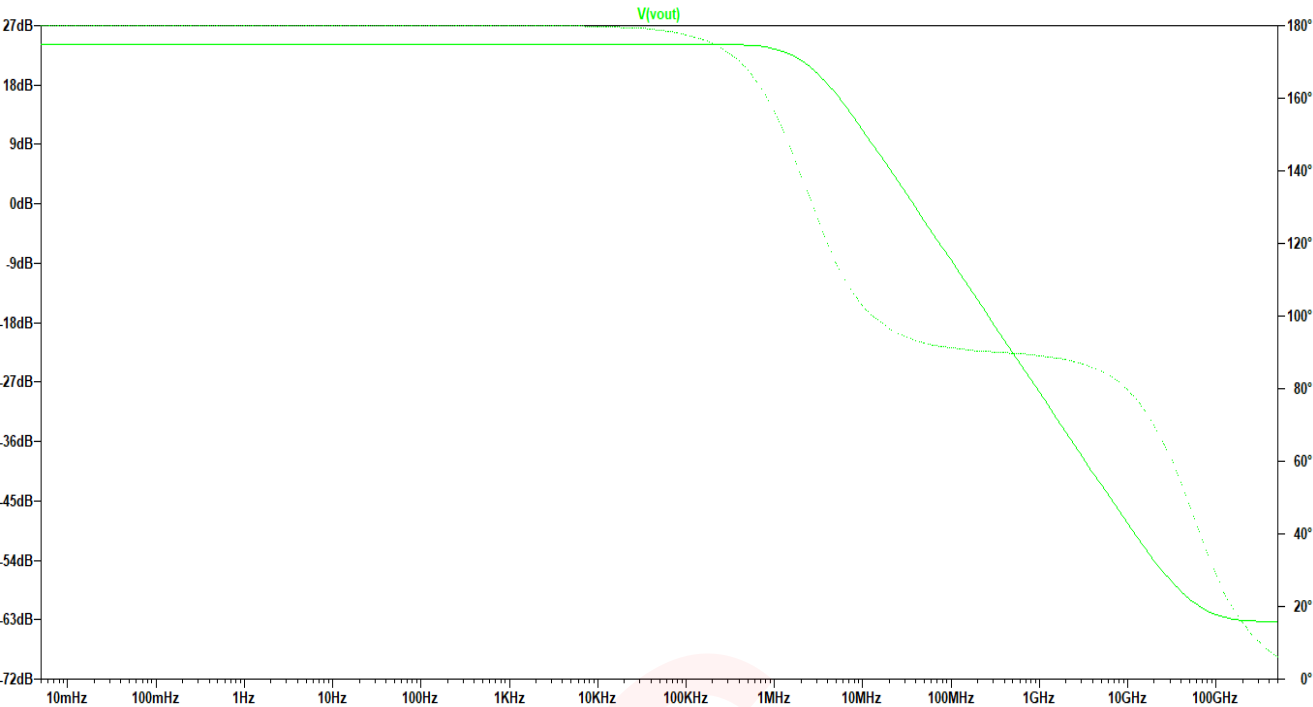


For bandwidth= $24.23 \text{ dB} - 3 \text{ dB} = 21.23\text{dB}$ For this see the frequency.


Tabulation-

Parameter	Calculated	Simulation
Gain	16.2	16.275 above
Gain in dB	24.19dB	24.23 dB (Fig 4)
Bandwidth	2.29 MHz	2.271 MHz (Fig 5)

b) Obtain the output voltage-

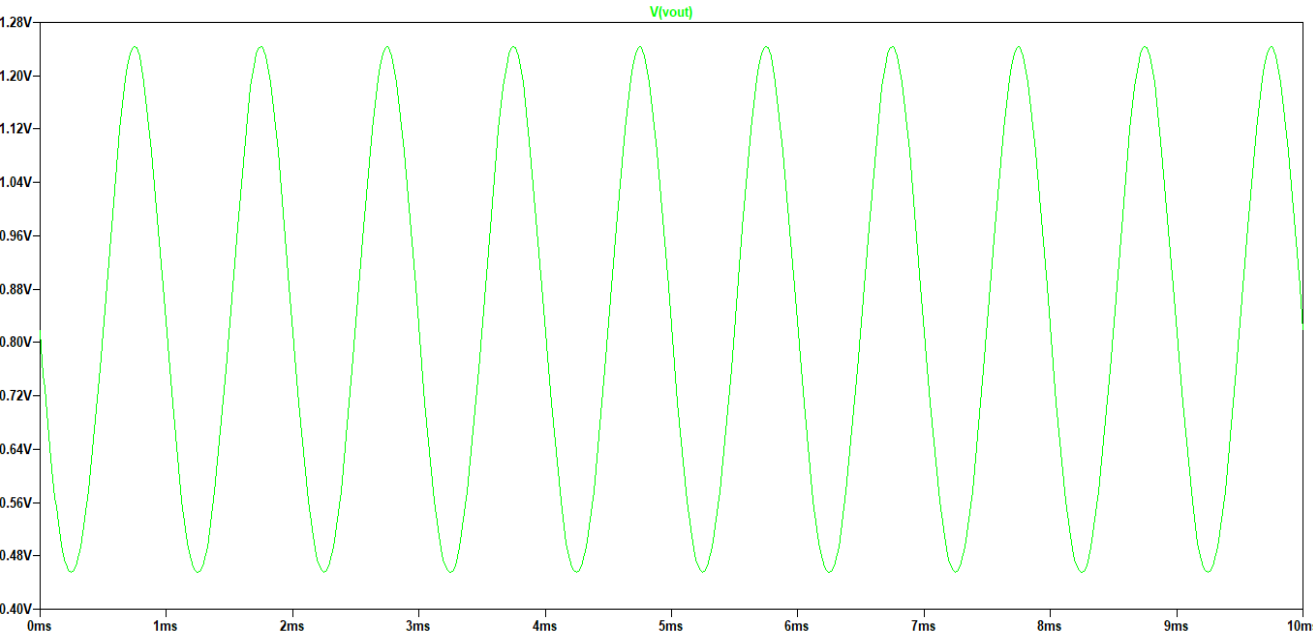

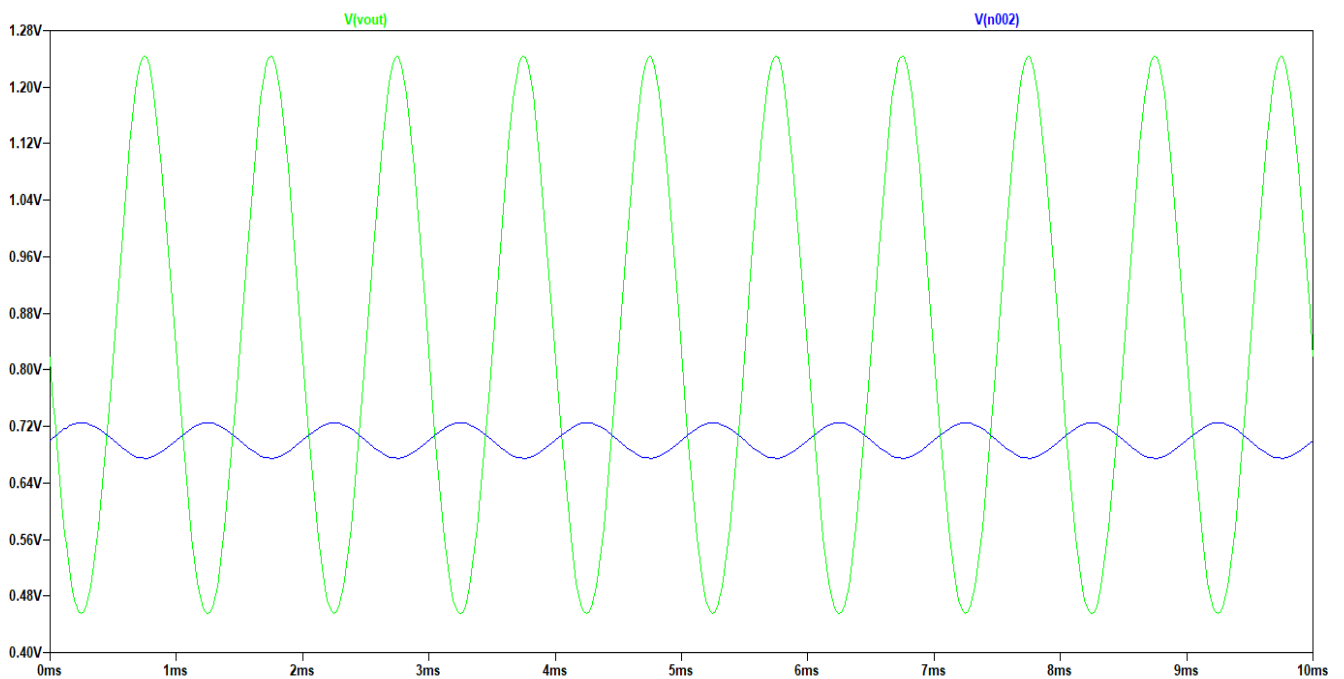Peak to peak= $1.243 \text{ v} - 0.455 \text{ v} = 0.788 \text{ volt}$



$$V_m(\text{output}) = [0.788/2] = 0.394 \text{ volt}$$


$$V_m(\text{input}) = [724\text{mv} - 675\text{mv}] / 2 = 0.0499 / 2 = 0.02495 \text{ volt}$$

$$\text{Gain} = 0.394 / 0.02495 = 15.8$$

$$20 \log 15.8 = 24 \text{ dB}$$


c) Repeat for 100 mVpp, 200 mVpp and 500 mVpp.

for 100 mv peak to peak

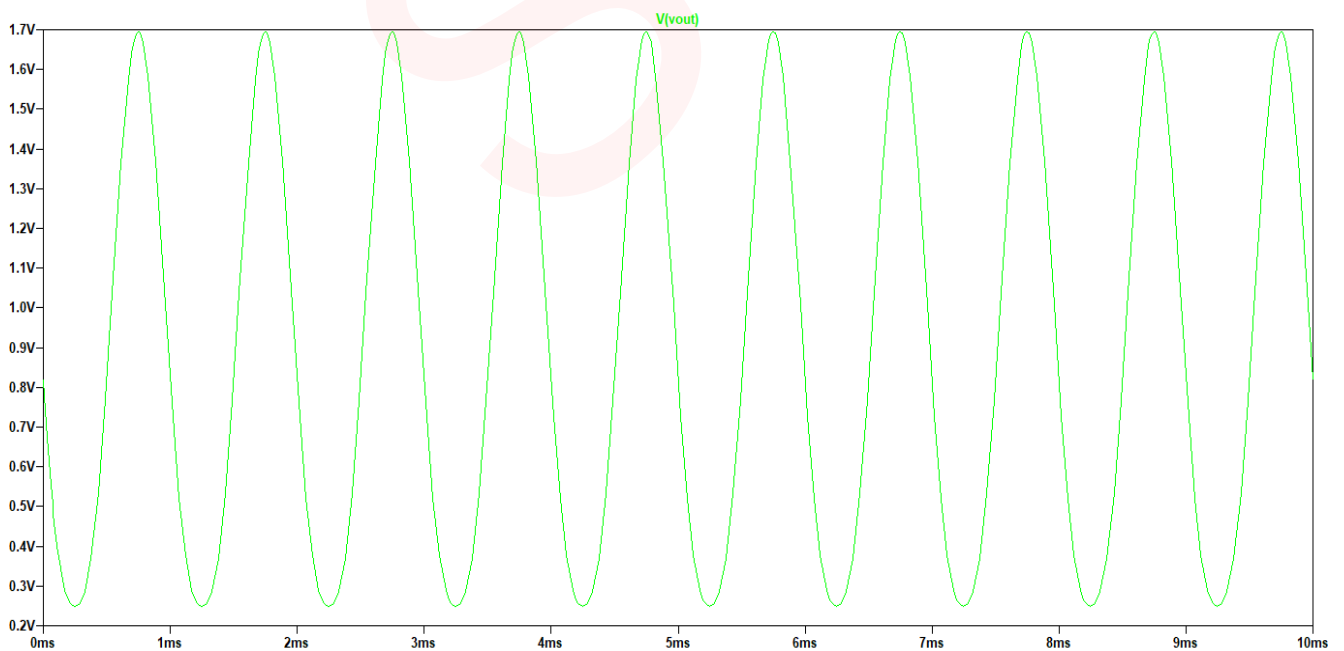


$$1.69 - 0.249 = 1.441 \text{ v}$$

For 200mv peak to peak

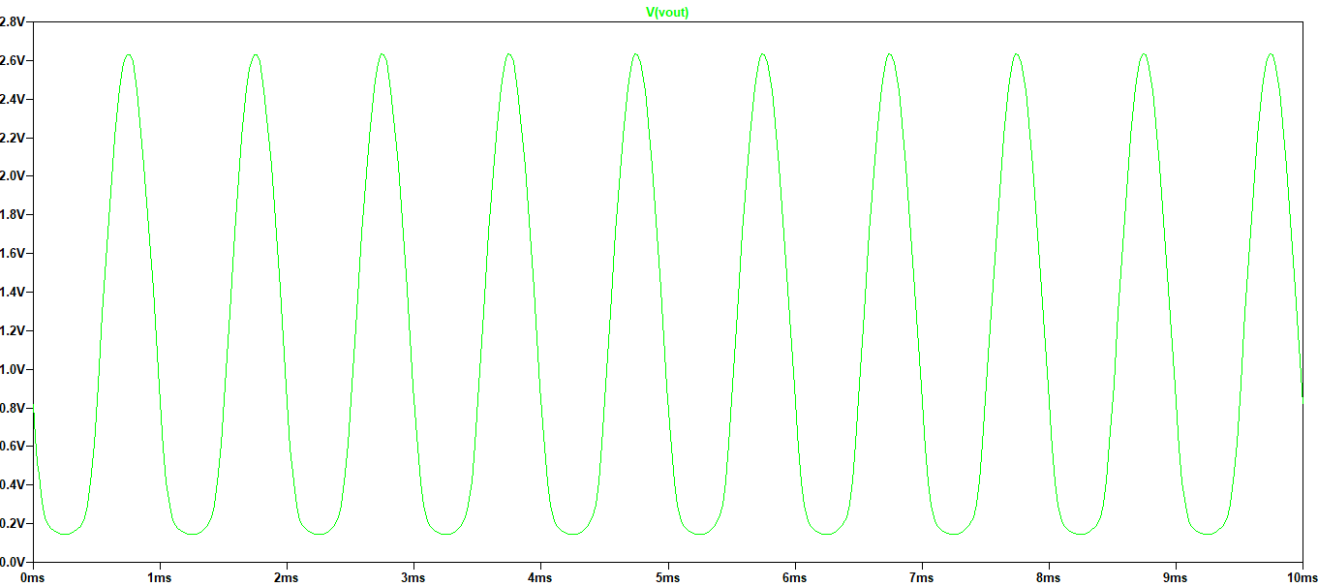

$2.63 - 0.145 = 2.631 \text{ volt}$

For 500mv peak to peak-

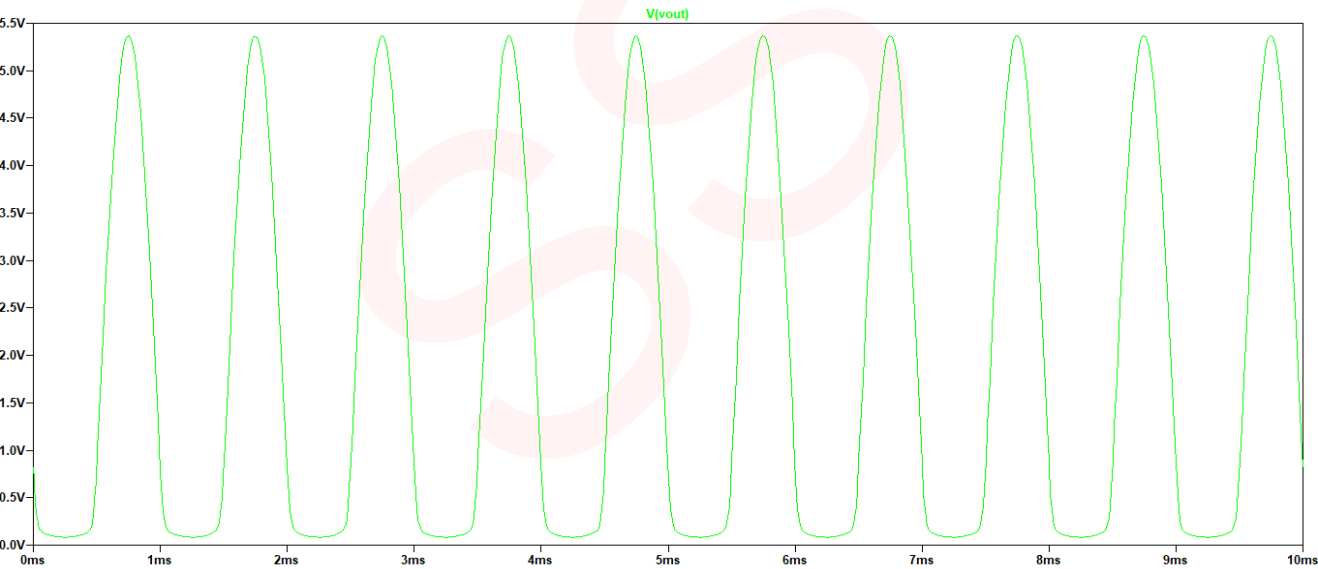

$5.36 \text{ v} - 84.26\text{mv} = 5.285 \text{ volt}$

d) 1 –dB Gain compression

```
Circuit: * C:\Users\DELL\AppData\Local\LTspice\Draft8.asc
Ignoring BSIM parameter XL
Ignoring BSIM parameter XW
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
Direct Newton iteration for .op point succeeded.
N-Period=1
Fourier components of V(vout)
DC component:0.834565

Harmonic      Frequency      Fourier      Normalized
Number        [Hz]          Component    Component
1             1.000e+3      3.882e-1     1.000e+0
2             2.000e+3      1.352e-2     3.482e-2
3             3.000e+3      6.726e-3     1.732e-2
4             4.000e+3      9.478e-4     2.441e-3
5             5.000e+3      4.295e-4     1.106e-3
6             6.000e+3      4.186e-4     1.078e-3
7             7.000e+3      3.471e-4     8.939e-4
8             8.000e+3      1.686e-4     4.343e-4
9             9.000e+3      6.670e-4     1.718e-3
10            1.000e+4      1.320e-4     3.399e-4
Partial Harmonic Distortion: 3.905394%
Total Harmonic Distortion: 3.920800%
```

$$\text{Fundamental component} = a_1 V_m + \frac{3}{4} a_3 V_m^3 = 3.882 \times 10^{-1} = 0.3882$$

$$\text{Third harmonic component} = \frac{1}{4} a_3 V_m^3 = 6.726 \times 10^{-3}$$

$$a_3 = 1721.85$$


$$a_1 = 14.72$$

$$\text{1-dB compression point} = \sqrt{0.145 \left| \frac{a_1}{a_3} \right|}$$

$$\text{1-dB compression point} = 0.035$$

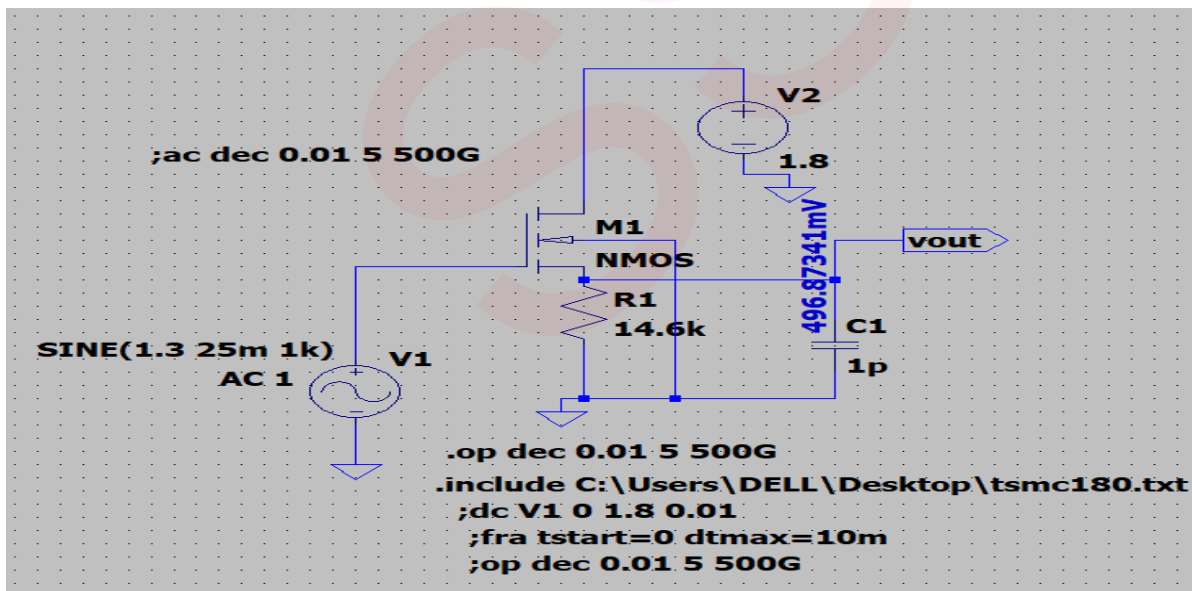3) Realize a NMOS CD amplifier using the same transistor designed (sized) in problem 1 above. Keep the same DC bias current. Set the input DC bias voltage to 1.3 V. Perform the following experiments on the designed amplifier.

= Earlier our DC bias current was $34\mu\text{A}$ so by calculating we get the source resistance as 14.6 Kohm



Circuit: * C:\Users\DELL\AppData\Local\LTspice\Draft9.asc

Ignoring BSIM parameter XL
 Ignoring BSIM parameter XW
 Warning: Pd = 0 is less than W.
 Warning: Ps = 0 is less than W.
 Direct Newton iteration for .op point succeeded.
 Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---

Name:	m1
Model:	nmos
Id:	3.40e-05
Vgs:	8.03e-01
Vds:	1.30e+00
Vbs:	-4.97e-01
Vth:	5.94e-01
Vdsat:	1.44e-01
Gm:	2.44e-04
Gds:	7.89e-06
Gmb:	5.49e-05

Calculation of gain for CD amplifier theoretically is shown below-

In CD amplifier body and source are not connected to each other so we have to take G_{mb} also in consideration.

$$\text{Total} = G_{mb} + G_{ds}$$

$$= 5.49 \times 10^{-5} + 7.89 \times 10^{-6} = 62.79 \times 10^{-6}$$

$$g_m = 2.44 \times 10^{-4}$$

Here: -

$$\begin{aligned} r_o &= \frac{1}{G_{mb} + G_{ds}} & g_m &= 2.44 \times 10^{-4} \\ &= \frac{1}{62.79 \times 10^{-6}} \\ &= 15.92 \text{ k}\Omega \\ R_D || r_o &= 14.6 \text{ k}\Omega || 15.92 \text{ k}\Omega \\ &= \frac{14.6 \text{ k}\Omega \times 15.92 \text{ k}\Omega}{14.6 \text{ k}\Omega + 15.92 \text{ k}\Omega} \\ &= 7.61 \text{ k}\Omega \\ A_v &= \frac{g_m (R_D || r_o)}{1 + g_m (R_D || r_o)} \\ &= \frac{2.44 \times 10^{-4} \times 7.61 \times 10^3}{1 + 2.44 \times 10^{-4} \times 7.61 \times 10^3} \\ &= \frac{1.856}{1 + 1.856} = 0.650 \end{aligned}$$

(a) Frequency response of the amplifier. Find the small signal DC gain and bandwidth of the amplifier. Compare with the values calculated using the small signal parameters obtained from the DC operating point simulation.

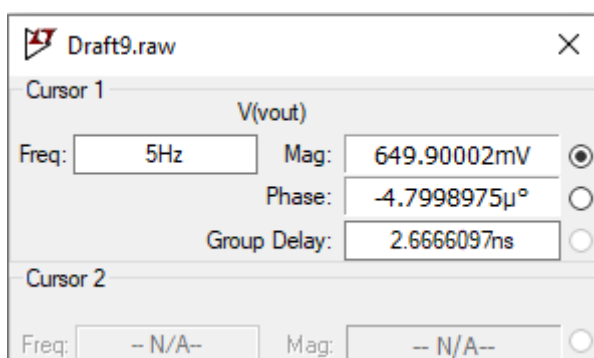


Fig 6



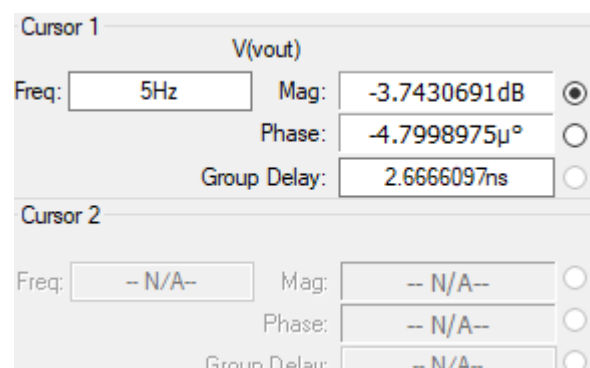


Fig 7

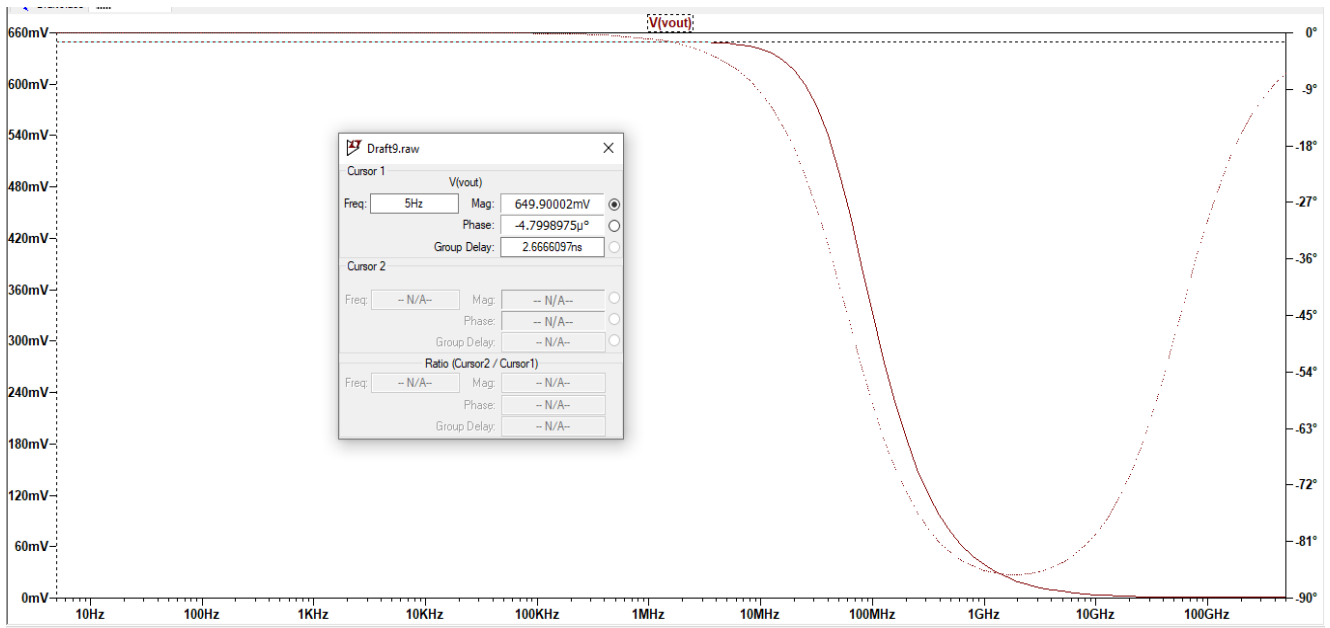

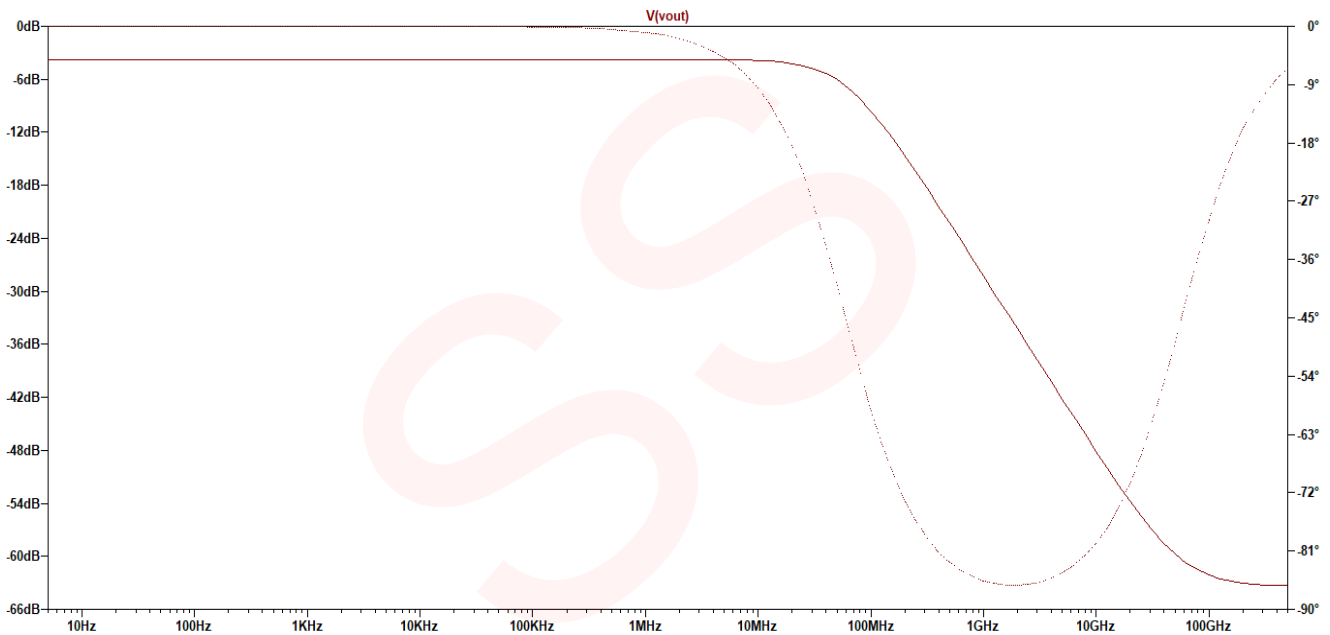The gain is coming out to be 0.649 which is same as 0.650



For bandwidth:

$$A_v = 20 \log(\text{gain})$$

$$= 20 \log(0.650) = -3.741 \text{ Decibel}$$

For Bandwidth: (Simulation)

$$\text{Gain in Db} - 3\text{dB} = -3.741 - 3 = -6.741 \text{ dB}$$

For 11.74 decibel the frequency is 59.14 MHz

$$\text{Bandwidth} = f_1 - f_2 = 59.14 - 0 = 59.14 \text{ MHz}$$


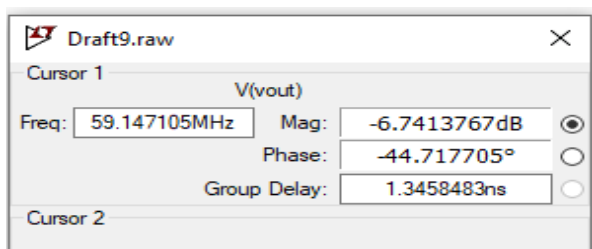


Fig 8

Tabulation-

Parameter	Calculated	Simulation
Gain	0.650	0.649 (Fig 6)
Gain in dB	-3.741 dB	-3.743 dB (Fig 7)
Bandwidth	59.14 MHz	59.14 MHz (Fig 8)

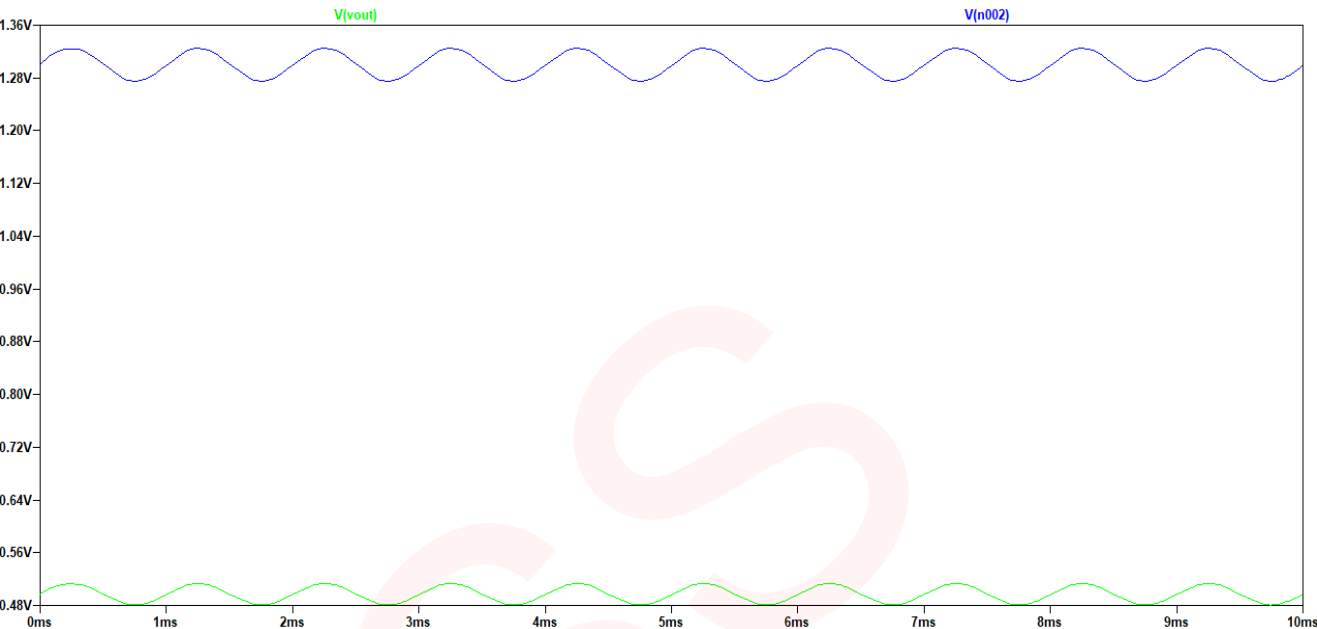b) Excite the amplifier with a 50 mV peak-to-peak sine wave of frequency 1 kHz riding on the input DC bias voltage and obtain the output. What is the peak-to-peak voltage of the output?



Blue one is for input and other one is for output.


Peak to peak output= 31.8 millivolt (Fig 9)

V_m (out)= 15.9 millivolt

V_m (in)=25 millivolt


$$\text{Gain} = \frac{V(\text{out})}{V(\text{in})} = \frac{15.9 \text{ mV}}{25 \text{ mV}} = 0.636$$

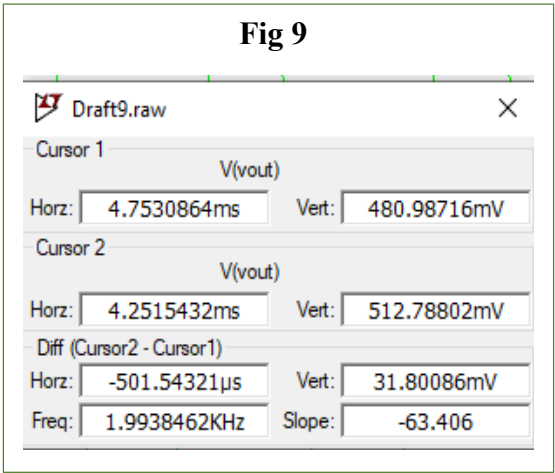The gain we can clearly see is same as calculated theoretically as well as frequency response.



C) Repeat the transient analysis by increasing the input to 100 mVpp, 200 mVpp and 500 mVpp. Obtain the output and note down the peak-to-peak voltage. What do you observe and why? How does the waveform compare with that of the CS amplifier? Comment on it.


For 100mV peak to peak input:

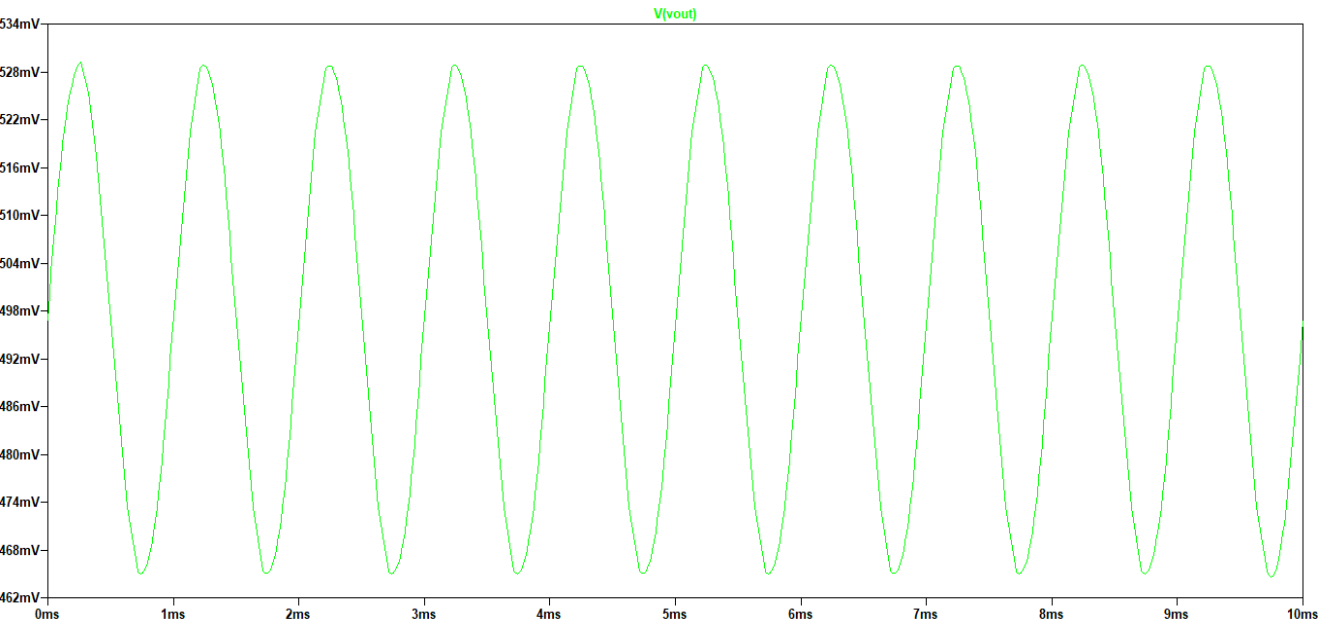

Peak to peak output voltage= 63.81 millivolt

Output voltage=31.905 millivolt

For 200mV peak to peak input:

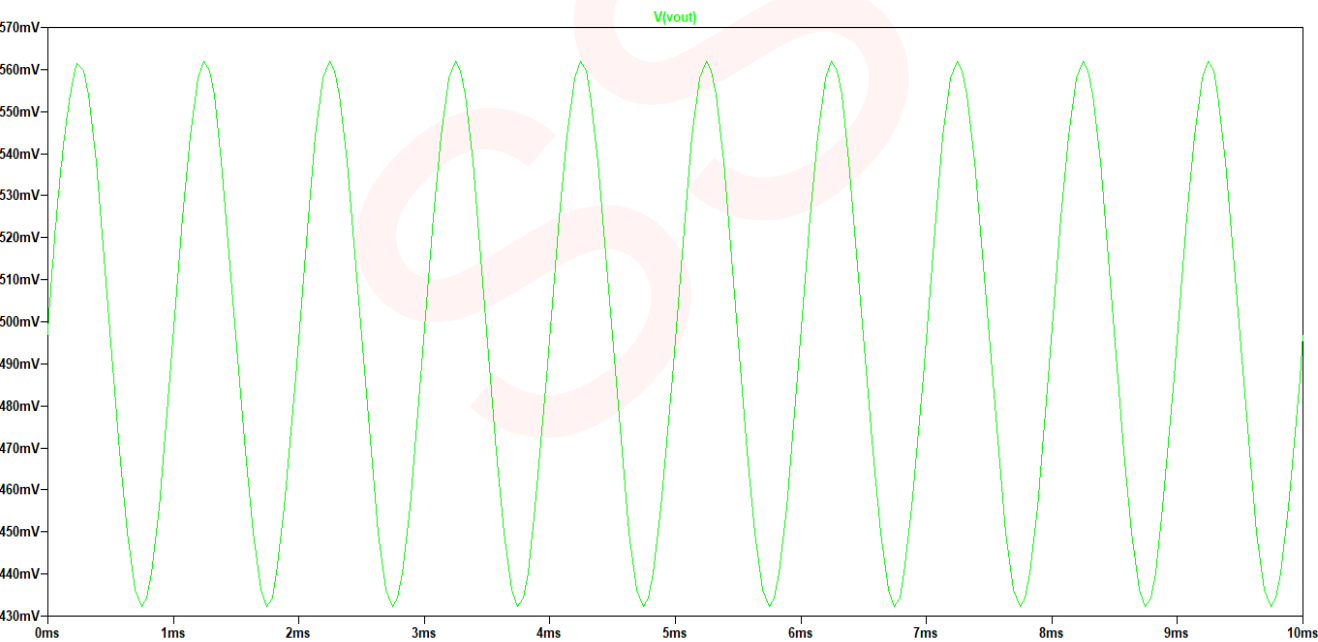


Peak to peak output voltage= 128.81 millivolt

Output voltage=64.4 millivolt

For 500 mV peak to peak input:


Peak to peak output voltage= 322.22 millivolt

Output voltage=161.11 millivolt

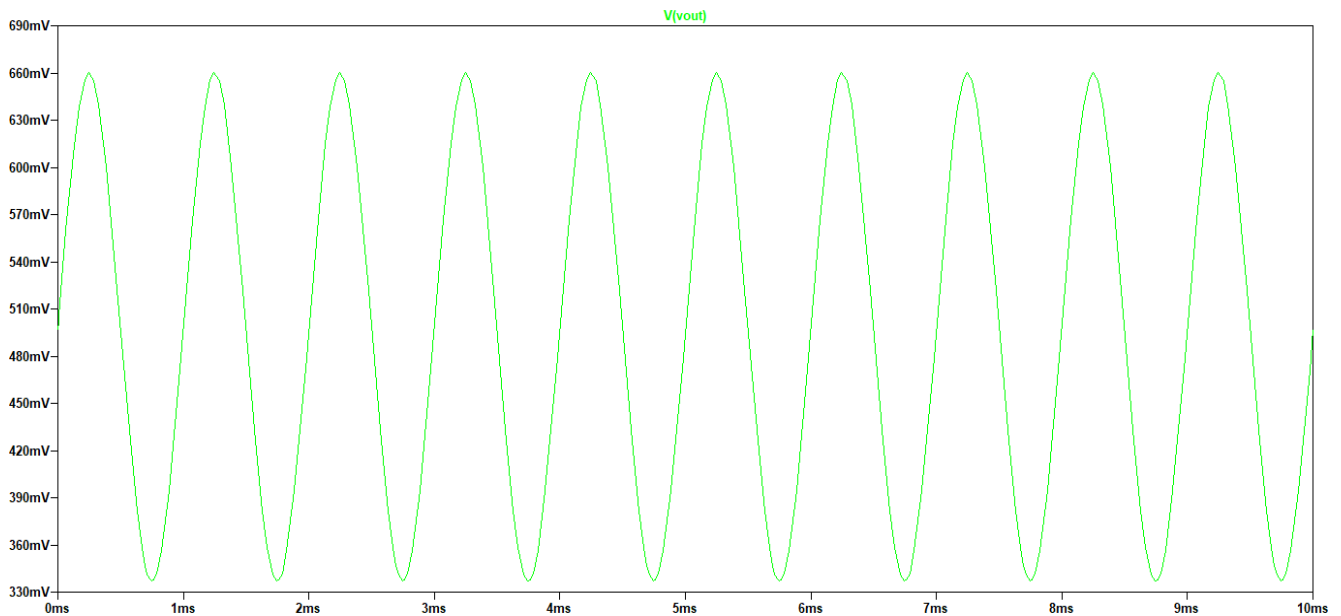

Obsevation-

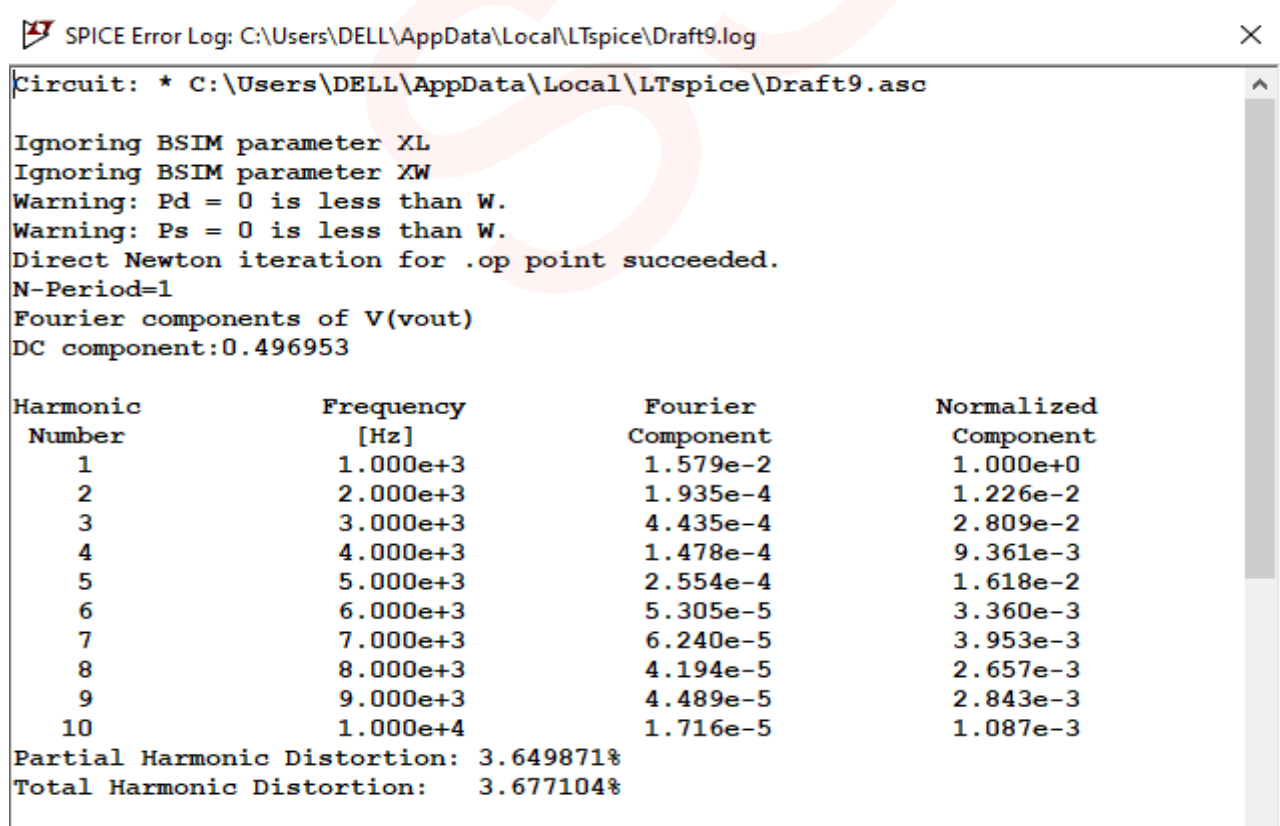d) Find the 1-dB compression point of the amplifier by performing total harmonic distortion (THD) analysis. How does it compare with the CS amplifier? Comment on it.



$$\text{Fundamental component} = a_1 V_m + \frac{3}{4} a_3 V_m^3 = 1.579 \times 10^{-2}$$

$$\text{Third harmonic component} = \frac{1}{4} a_3 V_m^3 = 4.435 \times 10^{-4}$$

$$a_3 = 113.536$$

$$A_1 = 0.5784$$

$$\text{1-dB compression point} = \sqrt{0.145 \left| \frac{\alpha_1}{\alpha_3} \right|}$$

$$\text{1-dB Compression point} = 5.335$$